

**University of Bahrain**  
**College of Information Technology**  
*Department of Computer Engineering*

**ITCE 202: Digital Logic**  
**Test II**

**Time: 1:00 hour**

**Date: December 14, 2004**

Question	Marks	Score
1	20	
2	20	
3	20	
4	20	
5	20	
Total	100	

ID. No.	Name:	Sec.:
---------	-------	-------

---

**Show all your work.**

---

**Q1 (20 points)**

A combinational Logic Circuit accepts two 4-bit binary numbers  $A = A_3 A_2 A_1 A_0$  and  $B = B_3 B_2 B_1 B_0$  and generates a single output Z such that:

$Z = 1$  if  $A + B + 7 \geq 12$  else  $Z = 0$

Use any necessary ICs and logic gates to implement the combinational circuit.




**Q2(20 points)**

Use 3-to-8 decoder(s) with enable to implement a code converter combination that takes as its inputs an Excess-3 code digit and outputs its equivalent BCD digit


 
**Q3(20 points)**

Express F in a S-O-P form (Do not simplify)



 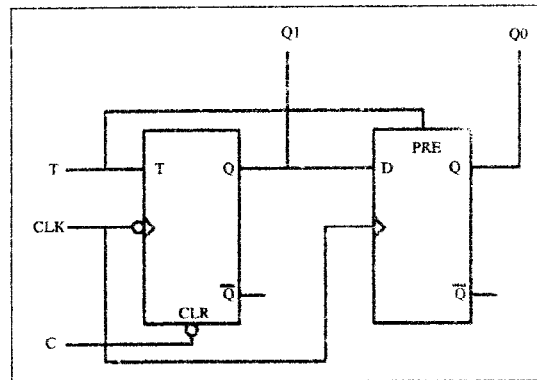**Q4(20 points)**

Complete the following timing diagram for the circuit shown below.



**Q5(20 points)**

A gated Latch has two inputs G, and L behaves as follows: If  $G = 0$  the latch does not change its state. If  $G=1$ , the next state of the latch is equal to its input L.

(a) Derive the characteristic equation of the G-L latch.

(b) Show how a J-K latch can be converted to a G-L latch.

